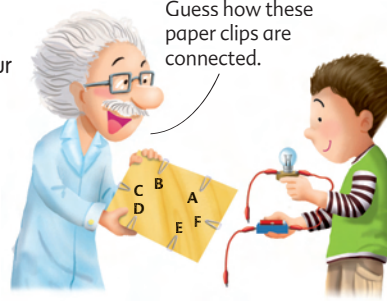





3. Flip the cardboard over so that your friend cannot see the connections you have made. Then get your friend to use the simple circuit to guess how the connections are made below the cardboard.

Guess how these paper clips are connected.




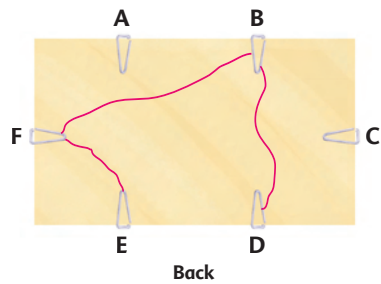Question

Get your friend to draw what he or she thinks is the connection you have made below your cardboard.



Your friend's guess

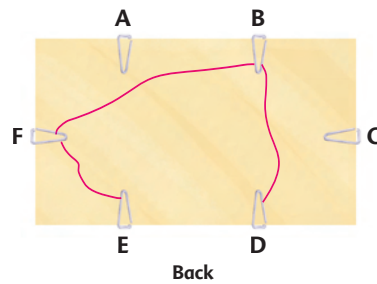

Your answer

Is your friend correct? Yes / No

Extension

Here is a card with some questions. Draw lines to show how the paper clips should be connected.

